

# **VHDL For Logic Synthesis (2)** **(Synthesizable Code)**

**Introduction to CAD**

***Naehyuck Chang***

`naehyuck@snu.ac.kr`

# Introduction

- Hardware implementation of VHDL code depends on
  - Coding conventions
  - Fitter technology
  - Optimization option
  - Nature of application
- Not all design can be synthesizable.

## Introduction (contd.)

- Not synthesizable VHDL code
  - High-level performance model
  - Test benches
  - Hardware/software mixed model
- Design for synthesis does require additional constraints.
  - Gated clock, timing characteristics, unbounded conditions, enumerated types, *etc.*

# Introducton (contd.)

- Optimization
  - Different target architecture: PLD versus FPGA
- Using constant or simple one-bit data types whenever possible.

# Combinational Logic

- Logical operators
  - and, or, nand, not, xor and not
  - Defined for bit and Boolean types.
  - Also defined for **std\_logic**, **std\_ulogic** and **std\_logic\_vector** when **ieee** library and **std\_logic\_1164** package are included.

# Combinational Logic (contd.)


- Example 1

```
entity logical_ops_1 is  
    port (a, b, c, d: in bit;  m: out bit);  
end logical_ops_1;
```

```
architecture example of logical_ops_1 is  
    signal e: bit;  
begin
```

```
    m <= (a and b) or e; --concurrent signal assignments  
    e <= c xor d;
```

```
end example;
```

 


# Combinational Logic (contd.)

 - Example 2

```
entity logical_ops_2 is  
  port (a, b: in bit_vector (0 to 3);  
        m: out bit_vector (0 to 3));  
end logical_ops_2;
```

```
architecture example of logical_ops_2 is  
begin  
  m <= a and b;  
end example;
```



# Combinational Logic (contd.)

- Relational operators

Operator	Description
=	Equal
/=	Not equal to
>	Greater than
<	Less than
>=	Greater than or equal to
<=	Less than or equal to




# Combinational Logic (contd.)

- Resulting type is Boolean.
- Equal operators are defined for all VHDL data types.
- Magnitude operators are defined for numeric types, enumerated types and some array.
- Overloaded version is defined for **bit\_vector** and **std\_logic\_vector** types.

# Combinational Logic (contd.)

 - Example 1


```
entity relational_ops_1 is  
    port (a, b: in bit_vector (0 to 3); m: out Boolean);  
end relational_ops_1;  
architecture example of relational_ops_1 is  
begin  
    m <= a = b;  
end example;
```



# Combinational Logic (contd.)

 - Example 2

```
entity relational_ops_2 is  
  port (a, b: in integer range 0 to 3; m: out Boolean);  
end relational_ops_2;  
architecture example of relational_ops_2 is  
begin  
  m <= a >= b;  
end example;
```



# Combinational Logic (contd.)

- Arithmetic operators

Operator	Description
++	Addition
=	Subtraction
*	Multiplication
/	Division
<b>mod</b>	Modulus
<b>rem</b>	Remainder
<b>abs</b>	Absolute Value
**	Exponentiation

# Combinational Logic (contd.)

- Operators are defined for numeric types.
- Overloaded version defines (+, -) operators for **bit\_vector** and **std\_logic\_vector** in the package **bit\_ops** and **std\_logic\_ops**.
- (+, -) operators are somewhat expensive.
- (\*, /, mod, rem) operators are **extremely** expensive.
  - Special optimization for a constant and an even power of 2.

# Combinational Logic (contd.)


- (abs) operator is cheap.
- (\* \*) operator only supports constant arguments.

# Combinational Logic (contd.)

- Example

```
package example_arithmetic is  
    type small_int is range 0 to 7;  
end example_arithmetic;  
  
use work.example_arithmetic.all;  
  
entity arithmetic is  
    port (a, b: in small_int; c: out small_int);  
end arithmetic;  
architecture example of arithmetic is  
begin  
    c <= a + b;  
end example;
```

# Combinational Logic (contd.)

 



# Combinational Logic (contd.)

- Shift operators

<b>Operator</b>	<b>Description</b>
sll	Shift Left Logical
srl	Shift Right Logical
sla	Shift Left Arithmetic
sra	Shift Right Arithmetic
rol	Rotate Left Logical
ror	Rotate Right Logical

# Combinational Logic (contd.)

- Operators are defined for `bit` and `Boolean` types.
- Overloaded version defines shift operators for **`bit_vector`** and **`std_logic_vector`** in the package **`std_logic_ops`**.
- Operators are not expensive the right operand is constant.
- Operators are quite expensive when the right operand depends on a signal.

# Conditional Logic

- Conditional logic is combinational logic that implements a multiplexer-like function.
- Two forms
  - Conditional signal assignment: if statement
  - Selected signal assignment: case statement

# Conditional Logic (contd.)

- Concurrent statement
  - Conditional signal assignment

```
entity control_stmts is  
    port (a, b, c: in Boolean; m: out Boolean);  
end control_stmts;
```

```
architecture example of control_stmts is  
begin  
    m <= b when a else c;  
end example;
```

# Conditional Logic (contd.)

- IEEE standard 1076-1993 describes that **else** clause is optional
  - Without **else** clause, the resulting circuit mostly introduces a latch, which may not be the desired circuit.

# Conditional Logic (contd.)

- Selected signal assignment


```
entity control_stmts is  
    port (sel: bit_vector (0 to 1); a,b,c,d: bit;  
          m: out bit);  
end control_stmts;  
  
architecture example of control_stmts is  
begin  
    with sel select  
        m <= c    when b"00",  
        m <= d    when b"01",  
        m <= a    when b"10",  
        m <= b    when others;  
end example;
```

# Conditional Logic (contd.)

- Sequential statement
  - If statement
    - Must evaluate a Boolean type.
 
# Conditional Logic (contd.)

```
entity control_stmts is  
  port (a, b, c: in Boolean;  m: out Boolean);  
end control_stmts;  
architecture example of control_stmts is  
begin  
  process (a, b, c)  
    variable n: Boolean;  
  begin  
    if a then  
      n := b;  
    else  
      n := c;  
    end if;  
    m <= n;  
  end process;  
end example;
```






# Conditional Logic (contd.)

## – Case statement

- VHDL requires that all the possible conditions be represented in the condition of a **case** statement.
- Use the **others** clause at the end of a case statement to cover any unspecified conditions.
- Since **std\_ulogic** and **std\_logic types** have nine possible values (instead of two possible values for bit types), you should always include an **others** clause when using these types.
 
# Conditional Logic (contd.)

```
entity control_stmts is  
  port (sel: in bit_vector (0 to 1); a,b,c,d: in bit;  
        m: out bit);  
end control_stmts;  
architecture example of control_stmts is  
begin  
  process (sel,a,b,c,d)  
  begin  
    case sel is  
      when b"00" => m <= c;  
      when b"01" => m <= d;  
      when b"10" => m <= a;  
      when others => m <= b;  
    end case;  
  end process;  
end example;
```



# Replicated Logic

- Function
- Procedure
- Loop statement
- Generate statement
  - Concurrent loop statement

# Replicated Logic (contd.)

- Functions
  - always terminated by **return** statement.
  - For both functions and procedures, the VHDL synthesizer will generate a block of logic for each instance (unique reference to) the function or procedure.

# Replicated Logic (contd.)

```
entity func is
  port (a: in bit_vector (0 to 2);
        m: out bit_vector (0 to 2));
end func;

architecture example of func is
  function simple (w, x, y: bit) return bit is
  begin
    return (w and x) or y;
  end;
begin
  process (a)
  begin
    m(0) <= simple(a(0), a(1), a(2));
    m(1) <= simple(a(2), a(0), a(1));
    m(2) <= simple(a(1), a(2), a(0));
  end process;
end example;
```

# Replicated Logic (contd.)

- Procedures
  - do not have a return value.
  - A return statement may also be used in a procedure, where it never returns a value.

# Replicated Logic (contd.)

```
entity proc is  
  port (a: in bit_vector (0 to 2);  
        m: out bit_vector (0 to 2));
```

```
end proc;
```

```
architecture example of subprograms is
```

```
  procedure simple (w, x, y: in bit; z: out bit) is
```

```
  begin
```

```
    z <= (w and x) or y;
```

```
  end;
```

```
begin
```

```
  process (a)
```

```
  begin
```


```
    simple(a(0), a(1), a(2), m(0));
```

```
    simple(a(2), a(0), a(1), m(1));
```

```
    simple(a(1), a(2), a(0), m(2));
```

```
  end process;
```

```
end example;
```

 

# Replicated Logic (contd.)

- Loop statement
  - If possible, loop ranges should be expressed as constants. Otherwise, the logic inside the loop may be replicated for all the possible values of the loop ranges.
  - Loop statements may be terminated with an **exit** statement



# Replicated Logic (contd.)

```
entity loop_stmt is
  port (a: in bit_vector (0 to 3);
        m: out bit_vector (0 to 3));
end loop_stmt;

architecture example of loop_stmt is
begin
  process (a)
    variable b:bit;
  begin
    b := 1;
    for i in 0 to 3 loop      -- no need to declare i
      b := a(3-i) and b;
      m(i) <= b;
    end loop;
  end process;
end example;
```

## Replicated Logic (contd.)

- Specific iterations of the loop statement may be terminated with the **next** statement.
  - Terminates the current iteration of a loop, then continues with the first statement in the loop.

```
for I in 1 to 8 loop
  next when COPY_ENABLE(I) = '0';
  A(I) <= B(I);
end loop;
```

# Replicated Logic (contd.)

- While statement
  - Supported by the synthesizer only when the termination can be determined at the time of synthesis.
  - Unconditioned loops are not synthesizable.

# Replicated Logic (contd.)

```
entity while_stmt is  
  port (a: in bit_vector (0 to 3);  
        m: out bit_vector (0 to 3));
```

```
end while_stmt;
```

```
architecture example of while_stmt is
```

```
begin
```

```
  process (a)
```

```
    variable b: bit;
```

```
    variable i: integer;
```

```
  begin
```

```
    i := 0;
```

```
    while i < 4 loop
```


```
      b := a(3-i) and b;
```

```
      m(i) <= b;
```

```
    end loop;
```

```
  end process;
```

```
end example;
```

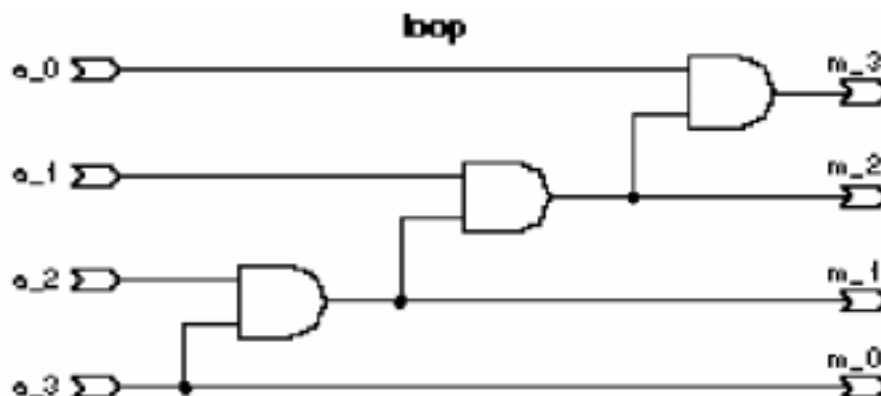

# Replicated Logic (contd.)

- Generate statement
  - Replicates one or more concurrent statements.
  - Has two forms: **for** and **if**.

```
Gen1: for i in 0 to 3 generate  
SM: mod1 port map(A(i),B(i),Y(i));  
end generate Gen1;  
  
SM(0): mod1 port map(A(0),B(0),Y(0));  
SM(1): mod1 port map(A(1),B(1),Y(1));  
SM(2): mod1 port map(A(2),B(2),Y(2));  
SM(3): mod1 port map(A(3),B(3),Y(3));
```

## Replicated Logic (contd.)

- If generate statement
  - describe a conditional selection of concurrent statements.

```
Gen2: if test_flag = 1 generate  
    test_pins <= current_state;  
end generate Gen2;
```

- the conditional expression (in this case "test\_flag = 1") must be a metalogic value (one that does not depend on a signal or variable.)

# Replicated Logic (contd.)

– Example:

```
for i in 0 to 3 generate  
  if i /= 2 generate  
    SM: mod1 port map A(i), B(i), Y(i);  
  end generate;  
end generate;
```

# Sequential Logic

- There is no
  - register assignment operator
  - special attributes or dot extensions for specifying clocks and resets.
- There are often several ways to describe a particular behavior. There is no right-style, however.
- Two commonly-used methods
  - `if-then` and `wait` statements



# Sequential Logic (contd.)

- Conditional specification
  - Relies on the inherent behavior of **if** statement.

```
process (clk)
begin
  if clk='1' then
    y <= a;
  else
    -- default: holds previous value
  end if;
end process;
```
  - ABEL-HDL makes the signal **zero** without **else** clause.

## Sequential Logic (contd.)

- If both condition has been written, the behavior would be **mux**.
- However, the following code results in error because **a** and **b** are not included in the **sensitivity list**.

```
process (clk)
  begin
    if clk='1' then
      y <= a;
    else
      y <= b;
    end if;
  end process;
```

# Sequential Logic (contd.)

- Inverting conditional logic

```
process (clk)
  begin
    if clk='1' then
      -- hold
    else
      y <= a;
    end if;
  end process;
```

```
process (clk)
  begin
    if clk='0' then
      y <= a;
    end if;
  end process;
```

# Sequential Logic (contd.)

- Rising-edge flip-flop

```
process (clk)
  begin
    if clk'event and clk='1' then
      y <= a;
    end if;
  end process;
```

# Sequential Logic (contd.)

- IEEE 1164 std\_logic (or std\_ulogic)
  - Improved accuracy of simulation.

```
process(clk)
  begin
    if rising_edge(clk) then
      y <= a;
    end if;
  end process;
```

# Sequential Logic (contd.)

- Caution
  - Checking **absence of clock edge** has no hardware counterpart.

```
Illegal      if (CLK_B'event and CLK_B = '1') then  --  
             C <= B;  
             end if;  
             end process;
```

# Sequential Logic (contd.)

- Do not assign a value in **false** branch
  - Also checks absence of clock edge

```
process (CLK)
begin
    if (CLK'event and CLK = '1') then
        SIG <= B;
    else
        SIG <= C;          -- Illegal
    end if;
end process;
```

# Sequential Logic (contd.)

- Summary
  - Incomplete **if** statement implies a flip-flop or latch primitive.
  - Incomplete assignments within **case** statements can also result in latches using combinational feedback rather than latch primitives.
  - Complete **if** statement specifies (using an **else** clause) a combinational function.



# Sequential Logic (contd.)

- The clock input (in this case **clk**) can have any other name.
- Implied flip-flops and latches can occur on either signals or variables.

# Sequential Logic (contd.)

- Wait statement

```
process  
    wait until expression;  
    .  
    .  
    .  
end process;
```

```
process  
    wait until clk'event and clk='1'  
    y <= a;  
end process;
```

## Sequential Logic (contd.)

- Suspends evaluation (over time) until an event occurs, and the expression evaluates to **true**.
- When used in a process, **no process sensitivity list** is required (or allowed).
- VHDL synthesizer limits that
  - **wait** statements must be located at either the beginning or end of a process.
  - There may not be more than one **wait** statement in a process.
- **Wait** statements are not recommended for use in synthesizable designs.

# Sequential Logic (contd.)

- Other examples of latches
  - Current conditional assignment

```
architecture dataflow of latch is  
begin  
    y <= a and b when clk else y;  
end dataflow;
```

# Sequential Logic (contd.)

## – Concurrent procedure call

```
architecture dataflow of flipflop is  
    procedure my_ff(signal clk,a,b: Boolean;  
        signal y : out Boolean)  
    begin  
        if clk='1' and clk'event then  
            y <= a and b;  
        end if;  
    end;  
begin  
    ff_1: my_ff (clock,input1,input2,outputA);  
    ff_2: my_ff (clock,input1,input2,outputB);  
end dataflow;
```

# Sequential Logic (contd.)

- Gated clock and clock enable
  - Gated clock
    - Unreliable and/or unsynthesizable

```
if clk='1' and clk1'event and ena then  
    q <= d;  
end if;
```

# Sequential Logic (contd.)

- Clock enable feature
  - By specifying in VHDL synthesizer.
  - Otherwise **mux** will be generated.

```
if clk='1' and clk1'event then  
    if ena then  
        q <= d;  
    end if;  
end if;
```

# Sequential Logic (contd.)

- Synchronous set/reset

```
process(clk)
begin
    if clk='1' and clk'event then
        if set='1' then
            y <= '1';
        else
            y <= a and b;
        end if;
    end if;
end process;
```



# Sequential Logic (contd.)

- Mixture of set/reset for an arbitrary encoding

```
process (clk)
begin
    if clk='1' and clk'event then
        if init='1' then
            y <= 7;          -- y is type integer
        else
            y <= a + b;
        end if;
    end if;
end process;
```

# Sequential Logic (contd.)

- Asynchronous set/reset

```
process (clk,reset)
begin
    if reset='1' then
        y <= false;           -- y is type Boolean
    elsif clk='1' and clk'event then
        y <= a and b;
    end if;
end process;
```